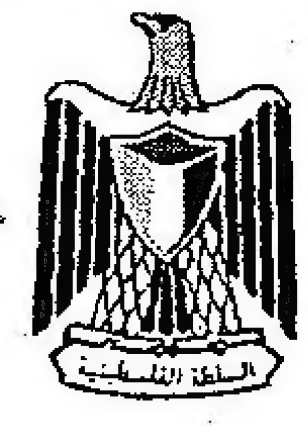


تم ارفعه  
بواسطة  
م. من  
الحوي عيسى

فيزياء (2)  
اصناف ثانيا

بسم الله الرحمن الرحيم



وزارة التربية والتعليم العالي  
Ministry of Education & Higher Education

السلطة الوطنية الفلسطينية  
Palestine national Authority

Palestine Technical University-Kadoorie	الاسم: <u>م. من</u>
Faculty of Applied Sciences	الرقم الجامعي: <u>22/25</u>
General Phys. II, Second Exam(Spring2010)	مدرس المادة: <u>د. صافي جبر</u>
Date: 17/05/2010 Time: 1 hour	الشعبة: <u>الفيزياء</u>

Note:  $1\mu = 10^{-6}$ ,  $1n = 10^{-9}$  (B)

Q1. Read the following carefully and circle the symbol of the most appropriate answer for each question. (1.5pt. for each of a 10 right answers)

1. Capacitance measures the ability of the capacitor to store:

- a) Charge on its surfaces; b) Electric energy between its surfaces;  
c) Electric field between its surfaces; d) All of the above.

2. An air-filled parallel-plate capacitor is fully charged by connecting it to a battery. When the capacitor is disconnected from the battery and a dielectric is inserted between its plates. Which quantity (quantities) remains (remain) the same?

- a) Its potential V; b) Its charge Q; c) Its capacitance C; d) All of them.

3. Three capacitors are connected as shown in Fig. (1), where  $C_1 = 2.0 \mu F$ ,  $C_2 = 1.0 \mu F$ ,  $C_3 = 3 \mu F$ . The equivalent capacitance (in  $\mu F$ ) between points a and b is

- a) 2; b) 0.75;  
c) 1.5; d) 8.

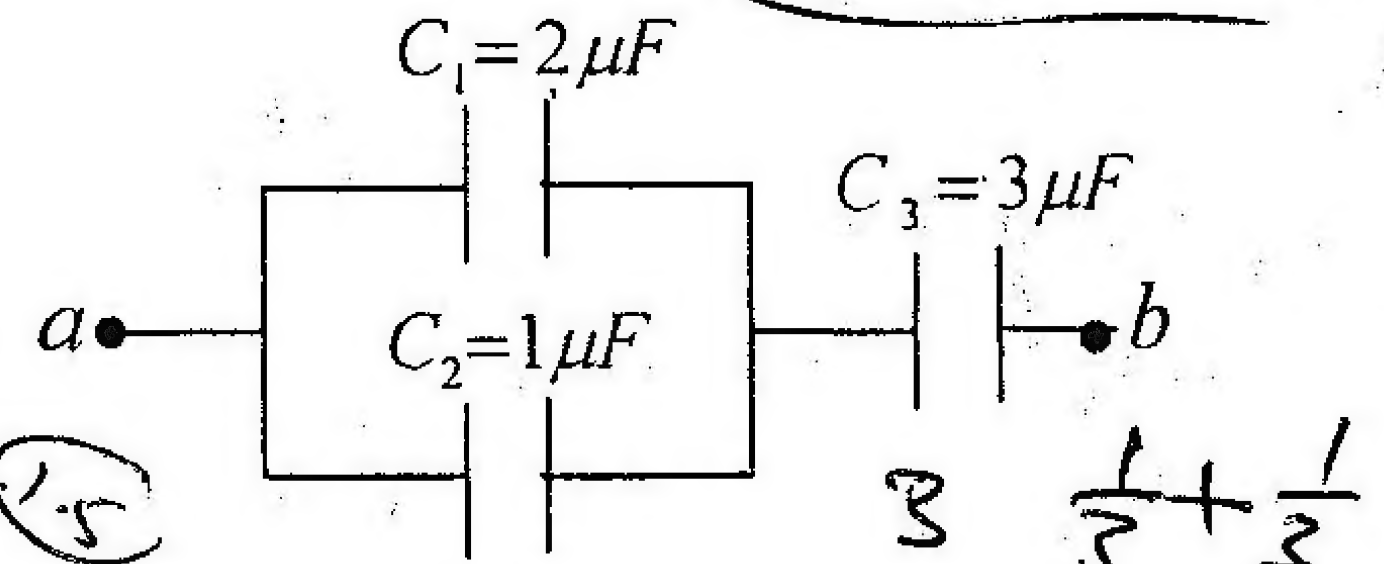


Fig.1

4. A  $4.0 \Omega$  resistor has potential drop of 8 V across its ends. The quantity of charge (in C) that pass through the resistor in 1 minute is

- a) 180; b) 3;  
c) 120; d) 30.

5. Electrical conductivity  $\sigma$  of a material depends on:

- a) the applied electric field. b) the geometry of the material;  
c) the current density in the material. d) physical quantities of the material;

6. The drift speed  $v_d$  in a material depends on:

- a) the current in the material; b) physical quantities of the material;  
c) the applied electric field; d) both b and c;

7. When charging a capacitor (Fig.2), the maximum current occurs

- a) at the time equal its time constant;  
b) at the moment the circuit is closed;  
c) after a long time;  
d) the current is constant, so no maximum occurs.

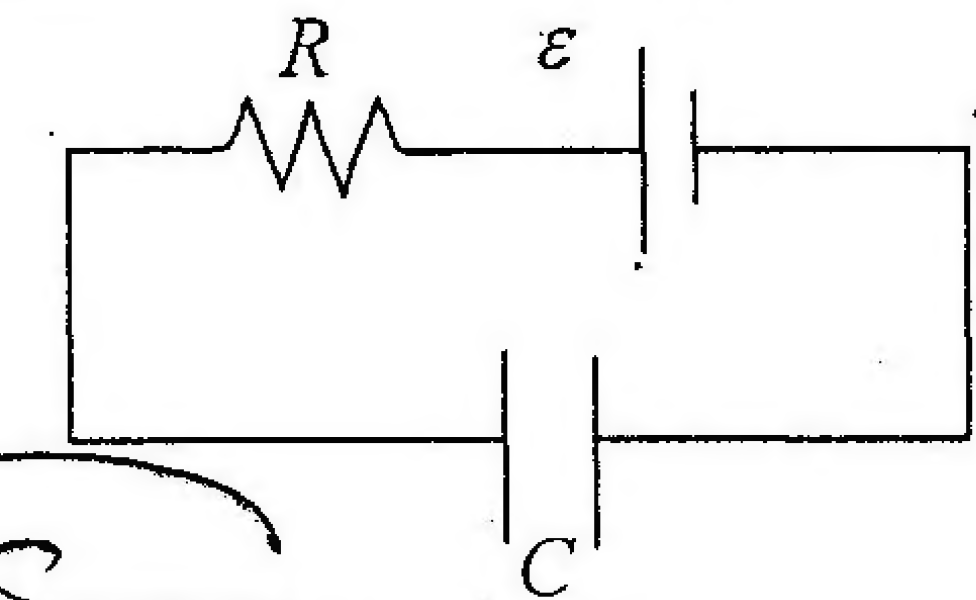


Fig.2

$$I(t) = \frac{\epsilon}{R} e^{-t/Rc}$$



$$\text{Energy in } P_s = 2 \times [\text{energy in Capacitor}]$$

8. In Q7 (directly above) the total energy delivered by the power supply in Fig. 2 is

- a)  $\frac{1}{2} C \epsilon^2$ ; b)  $2 C \epsilon^2$ ; c)  $C \epsilon^2$ ; d)  $\frac{1}{2} \epsilon C^2$ .

9. The time constant in an RC circuit is the time at which

- a) the energy stored becomes  $1/e$  of its final value;  
 b) the current decreases to  $1/e$  of its initial value;  
 c) a and b;  
 d) the charge becomes  $1/e$  of its final value.

$$\tau = RC$$

$$q(t) = 0$$

$$i(t) = 0.368 \left( \frac{\epsilon}{R} \right)$$


$$q(t) = 0.632 C \epsilon$$

10. Kirchhoff's first rule for currents at a junction is a statement of

- a) conservation of energy;  
 b) conservation of mass;  
 c) conservation of momentum;  
 d) conservation charge.

11. In Fig. (3), suppose that the switch has been closed for a long time sufficiently long for the capacitor to become fully charged, the charge  $Q$  on the capacitor (in  $\mu C$ ) is.

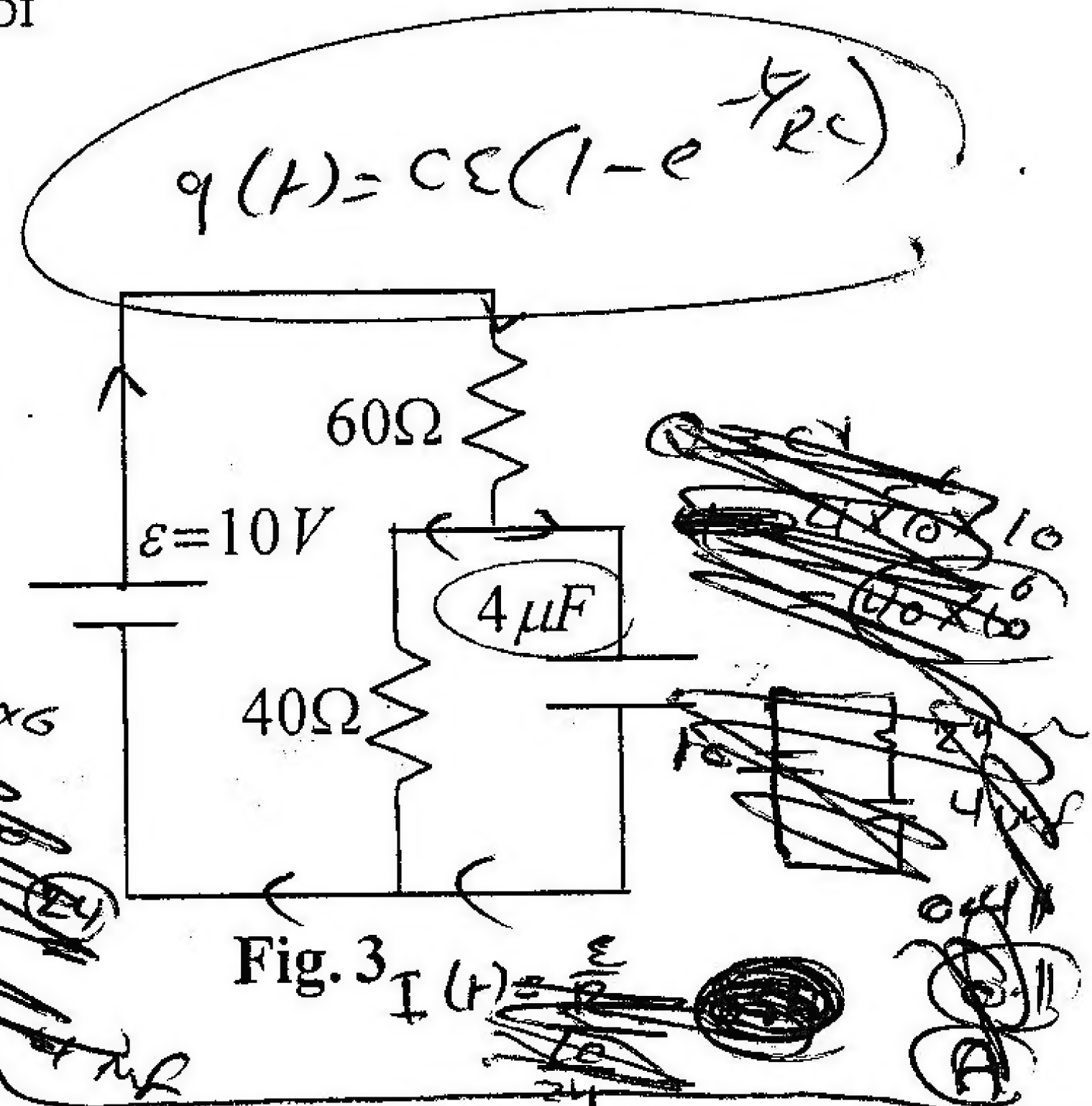- a) 28; b) 12; c)  $40 \times 10^{-6}$ ; d) 16;



Q2. In Fig. 4, the current through the resistor  $R_2$  is  $I = 2A$ ,

- a) What is the value of the currents  $I_1$  and  $I_2$ ? (5pts)  
 b) What is the value of  $\epsilon_2$ ? (3 pts)  
 c) What is the power dissipated in the  $3\Omega$  Resistor? (2 pts)

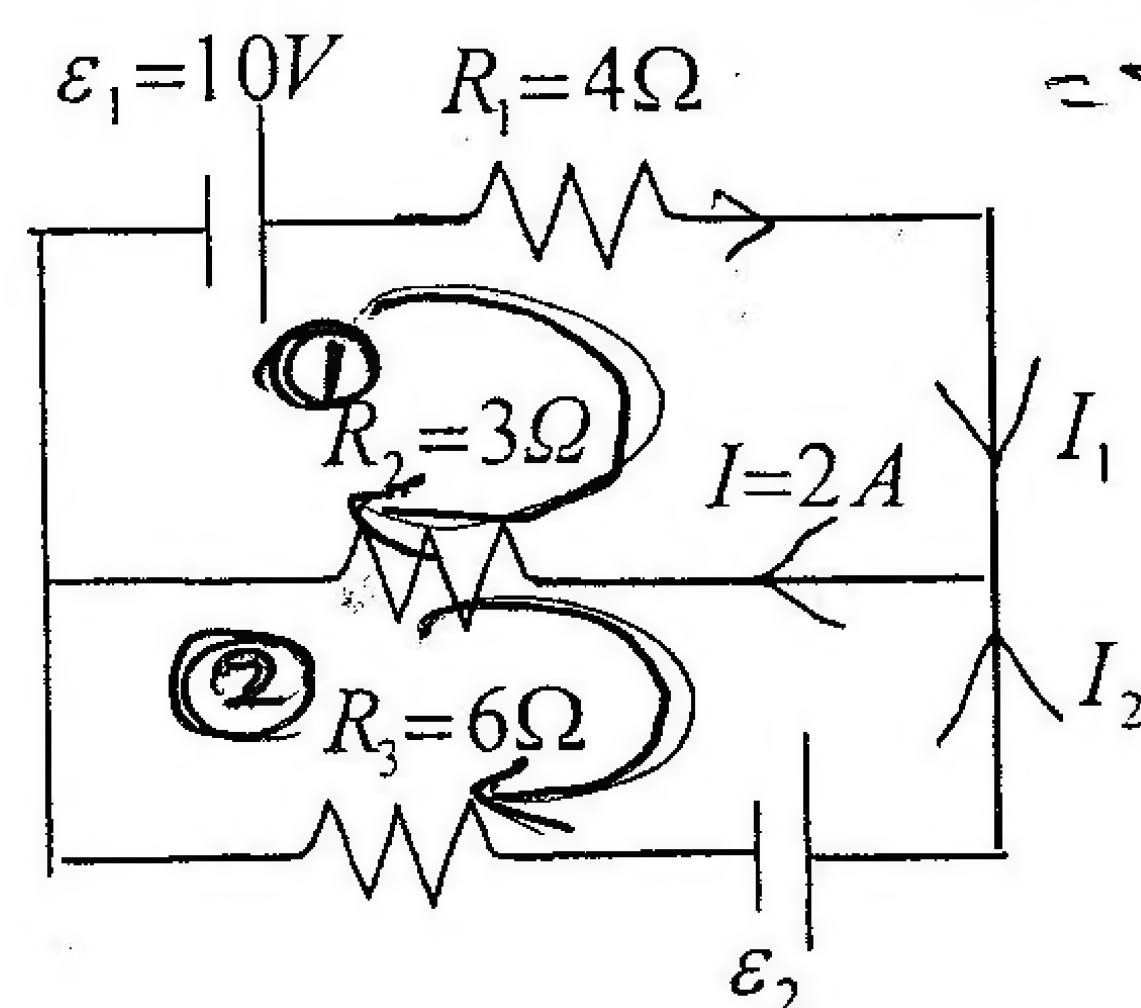


Fig. 4

a) Loop (1) - apply Kirchhoff's Laws

$$10 - 4I_1 - 3(2) = 0$$

$$10 - 6 - 4I_1 = 0$$

$$4 - 4I_1 = 0 \Rightarrow 4 = 4I_1 \Rightarrow$$

$$I_1 = \frac{4}{4} = 1A$$

$$I_1 + I_2 = 2$$

$$1 + I_2 = 2 \Rightarrow I_2 = 1A$$

b)

Loop (2) :-

$$3(2) - \epsilon_2 + 6(1) = 0$$

$$6 - \epsilon_2 + 6 = 0$$

$$\epsilon_2 = 12V$$

c) Power dissipated in the  $3\Omega$  Resistor =  $I^2 R = (2)^2 (3) = 12 \text{ Watt}$

$$\begin{aligned} I_1 &= 1A \\ I_2 &= 1A \\ \epsilon_2 &= 12V \\ P_{3\Omega} &= 12 \text{ Watt} \end{aligned}$$

End of the questions- Good Luck